

What TRS-80, LNW 80, Video-Genie, Atom, Junior Computer, Ohio owner has never dreamed of being able to connect some specialized circuit to his computer? And what about a design borrowed from another member of his micro computer club? Just think of the possibilities that opens up. That would have to be very complicated, you say. Not necessarily . . . read on and find out more.

bus extension

for the TRS-80 and other personal computers

It is no secret to anybody that there is a price war raging in the market for home computers. Every manufacturer tries to establish as wide a range as possible in order to sell the maximum number of extensions (their prices have fallen also, but not to the same extent as the actual computers). This can make it difficult to connect peripherals

to a computer without having to buy as many connectors and cables as circuits. When we came up against this problem we decided it was time to see how the Elektor bus board could be used with other (non-Elektor) equipment. Many specialized shops (and magazines) supply all sorts of different equipment, and

Table 1

| ACORN ATOM | TRS 80 MI LNW 80/I Video Genie I/II | 6809 | Z80 | 6502 | SC/MP INS 8060 INS 8070 | (seen from below) | SC/MP INS 8060 INS 8070 | 6502 | Z80 | 6809 | TRS 80 MI LNW 80/I Video Genie I/II | ACORN ATOM |
|---------------|---|-------|------------------------|-------|-------------------------------|-------------------------|-------------------------------|----------|-------|--------------------|---|---------------|
| +5 V | +5 V | +5 V | +5 V | +5 V | +5 V | 1. c | +5 V | +5 V | +5 V | +5 V | +5 V | +5 V |
| NC | NC | NC | NC | NC | 0E00-0FFF ¹⁾ | 2. a | NC | NC | NC | NC | NC | BLK0 |
| ↓ | (-12 V) | -12 V | -12 V | -12 V | -12 V | 3. b | -12 V | -12 V | -12 V | -12 V | (-12 V) | (-12 V) |
| RDY | WAIT | MRDY | WAITEX | RDY | N HOLD | 4. c | ↓ | RES | ↓ | RESET | SYSRES | NRST |
| NC | NC | NC | NC | NC | 0800-09FF ¹⁾ | 5. a | NRST | NC | PWCL | NC | NC | NC |
| D0 | DB00 | DB00 | DB00 | DB00 | DB00 | 6. b | NBREQ | NC | NC | DMA/BREQ | NC | NC |
| D2 | DB02 | DB02 | DB02 | DB02 | DB02 | 7. c | DB01 | DB01 | DB01 | DB01 | DB01 | D1 |
| D4 | DB04 | DB04 | DB04 | DB04 | DB04 | 8. a | DB03 | DB03 | DB03 | DB03 | DB03 | D3 |
| D6 | DB06 | DB06 | DB06 | DB06 | DB06 | 9. b | DB05 | DB05 | DB05 | DB05 | DB05 | D5 |
| NC | NC | HALT | NC | NC | CONT ¹⁾ | 10. c | DB07 | DB07 | DB07 | DB07 | DB07 | D7 |
| NMI | NC | NMI | NMI | NMI | SA | 11. a | NENIN | DD (OSI) | BUSRQ | NC | TEST | NC |
| NC | IN | NC | NC/BB2.4 ⁴⁾ | NC | SIN ¹⁾ | 12. b | S8 | IRQ | INT | IRQ | INT | IRQ |
| SO | NC | NC | NC | SO | F0 | 13. c | SOUT ¹⁾ | NC | NC | NC | OUT | NC |
| NC | NC | NC | NC | K6 | F2 | 14. a | F1 | K7 | NC | NC | NC | NC |
| ↓ | ↓ | ↓ | ↓ | ↓ | ↓ | 15. b | 0400-05FF ²⁾ | K5 | NC | NC | NC | NC |
| NC | NC | +12 V | +12 V | +12 V | +12 V/NC | 16. c | ↓ | ↓ | ↓ | ↓ | ↓ | NC |
| NC | NC | BA | BUSAK | K3 | NENOUT | 17. a | NC ²⁾ | K4 | NC | BS ²⁾³⁾ | NC | NC |
| A14 | AD14 | AD14 | AD14 | AD14 | AD14 | 18. b | NC/-5 V | -5 V | -5 V | -5 V | (-5 V) | (-5 V) |
| A12 | AD12 | AD12 | AD12 | AD12 | AD12 | 19. c | AD15 | AD15 | AD15 | AD15 | AD15 | A15 |
| A10 | AD10 | AD10 | AD10 | AD10 | AD10 | 20. a | AD13 | AD13 | AD13 | AD13 | AD13 | A13 |
| A8 | AD08 | AD08 | AD08 | AD08 | AD08 | 21. b | AD11 | AD11 | AD11 | AD11 | AD11 | A11 |
| A6 | AD06 | AD06 | AD06 | AD06 | AD06 | 22. c | AD09 | AD09 | AD09 | AD09 | AD09 | A9 |
| A4 | AD04 | AD04 | AD04 | AD04 | AD04 | 23. a | AD07 | AD07 | AD07 | AD07 | AD07 | A7 |
| A2 | AD02 | AD02 | AD02 | AD02 | AD02 | 24. b | AD05 | AD05 | AD05 | AD05 | AD05 | A5 |
| A0 | AD00 | AD00 | AD00 | AD00 | AD00 | 25. c | AD03 | AD03 | AD03 | AD03 | AD03 | A3 |
| NC | NC | AD01 | AD01 | AD01 | AD01 | 26. a | AD01 | AD01 | AD01 | AD01 | AD01 | A1 |
| NC | NC | E | MREQ | NC | NWDS+NRDS | 27. b | Φ2 | PHIEX | E | Φ | Φ | Φ2 |
| R/W | RAS | NC | RAS | K2 | 0A00-0BFF ¹⁾ | 28. c | NC | NC | NC | NC | NC | NC |
| NC | NC | NC | M1 | R/W | CE RAM | 29. a | K1 | NC | NC | NC | INTAK | NC |
| NC | NC | NC | IORQ | EX | CARDEN | 30. b | Φ1 | RFRSH | Q | Q | NC | SYNC |
| NRDS | RD | E R/W | RD | NC | NRDS | 31. c | RAM-R/W | WR | R/W | R/W | WR | NWDS |
| ↓ | ↓ | ↓ | ↓ | ↓ | ↓ | 32. a | ↓ | ↓ | ↓ | ↓ | ↓ | ↓ |

Notes:

1) not used by INS 8070

2) 15a reserved for A17

17a reserved for A16


3) subject to change

4) BB 2.4 = battery back-up + 2.4 V

These pin designations are the universally accepted standards (taking note 3 into account, of course).

83135

Figure 2. This shows an example of how the bus extension can be adapted for a TRS-80. Some of the a and c pins are connected together in this design to reduce resistance in the power supply lines (earth, +5 V and -12 V).

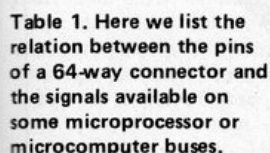

Note:
* indicates negative logic (an input or output is 'true' at the low logic level)
1 CAS for the 1 NW 80

each circuit is more sophisticated than the next. The very sight of them is enough to bring out the 'experimenter' in every one of us. To make proper experimentation feasible, what is really needed is a bus board, which has several connectors to accept one or a number of cards, and preferably with its own on-board supply.

Obviously everybody could design their own bus, to suit their own particular needs, but this would almost certainly rule out the possibility of borrowing a circuit from somebody else with a similar computer.

This is why Elektor designed a bus board in mid 1978 for the first microprocessor to appear in any of our circuits, the SC/MP. Gradually, as new micros started to appear (the 6502, Z80 and 6809), the number of lines needed began to increase. Originally the bus was intended only for one computer, the SC/MP. Eventually the Junior Computer arrived and the bus was used for this also. As the TRS-80 is still a very popular micro we decided that some rationalization was in order to make it compatible with the Elektor bus. The same applies for several other computers and the most recent addition to our list is the Acorn Atom.

What we have in mind is more than simply a modified and renewed bus. Since its inception, about five years ago, many micro computer buffs have used the Elektor bus for their computer system, whether that is Elektor's SC/MP or Junior Computer or something completely different. The layout suggested here has the advantage that it allows almost all the cards published by Elektor to be used without any modification; cards published elsewhere will also fit the format defined by the bus. Some of our cards have proved very popular, among them the universal memory card, the EPROM programmer and the floppy disk interface. Depending on what microprocessor the system is based on, the various cards can be used either without modification (6502), or with a certain number of modifications for some of them (Z80). Most of the Elektor cards can very easily be adapted to almost any system. Table 1 is a summary of the conventions used by various systems.

This extension can be used with any personal computer (possibly with some modification with some of those we have not mentioned), but it is *absolutely imperative* that the output bus of the computer is buffered (with a 74LS367 in the case of the TRS-80 model I).

It would be impossible to try to list all the possible circuits that could be plugged into the connectors of this bus extension. Some of the more interesting are: a speech synthesizer (SC01), sound synthesizer (1...3 AY-5-8910), EPROM programmer, all sorts of converters, real-time clock, circuit emulator. Often these various circuits have a large current consumption so it is a good idea to give the bus extension its own supply so that it can cope with these power-hungry cards. Circumstances dictate the characteristics of the supply (+ and -5 V, + and -12 V).

If such a supply is added only the earth line should be connected to the computer because the voltages supplied by the regulators will probably be slightly different and this could cause problems.

Nothing is more descriptive than an example, and we chose the TRS-80 as our guinea-pig. The signals available at the TRS-80 keyboard output connector are given in figure 1. The corresponding connections on the bus extension are illustrated in the drawing of figure 2.

Using this example you should be able to adapt this extension to any computer with a buffered output bus.

The simplest way of making this bus extension is to use a suitable printed circuit board, either the one described in the article 'new bus board for microprocessors' (January 1980, page 1-31), or the one described elsewhere in this issue. In the first case up to five connectors can be used, in the second this goes up to seven. In either case it is important that the components should be carefully located on the plug-in cards, to ensure that they can all be fitted.